

# COMMON SOURCE AMPLIFIER

## Specification:

Gain( $A_v$ )=40

$R_{out}$ =150 K $\Omega$

BW=25 MHz

## Calculation:

### Formula Used


- $BW(3dB \text{ freq}) = \frac{1}{2\pi \cdot R_{out} \cdot C_L}$        $A_v = g_m \cdot R_{out}$
- $R_{out} = r_{o1} // r_{o2}$
- $C_L = 42.44 \text{ fF}$
- $g_m / I_D = 10$  (Choose)
- $g_m = 0.266 \text{ mS}$
- $I_D = 26.6 \mu A$
- $g_m / g_{ds} = 81.72$  .....from chart       $I_D / W = 13.6$
- $g_{ds} = 3.25 \mu S$        $W_1 = 1.95 \mu m$
- $R_{o1} = 307.21 \text{ K}\Omega$        $V_{gs1} = 657.8 \text{ mV}$

Continue....

- $R_{o2}=293.12 \text{ K } \Omega$
- $g_{ds2}=3.41 \text{ } \mu\text{S}$
- $(I_d/g_{ds})_2=7.8$
- $(g_m/i_d)_2= 7.106 \text{ ..... from chart}$
- $(I_d/w)_2=7.312 \text{ ..... from chart}$
- $V_{gs2}=712.9 \text{ mV}$
- $W_2= 3.63 \text{ } \mu\text{m}$
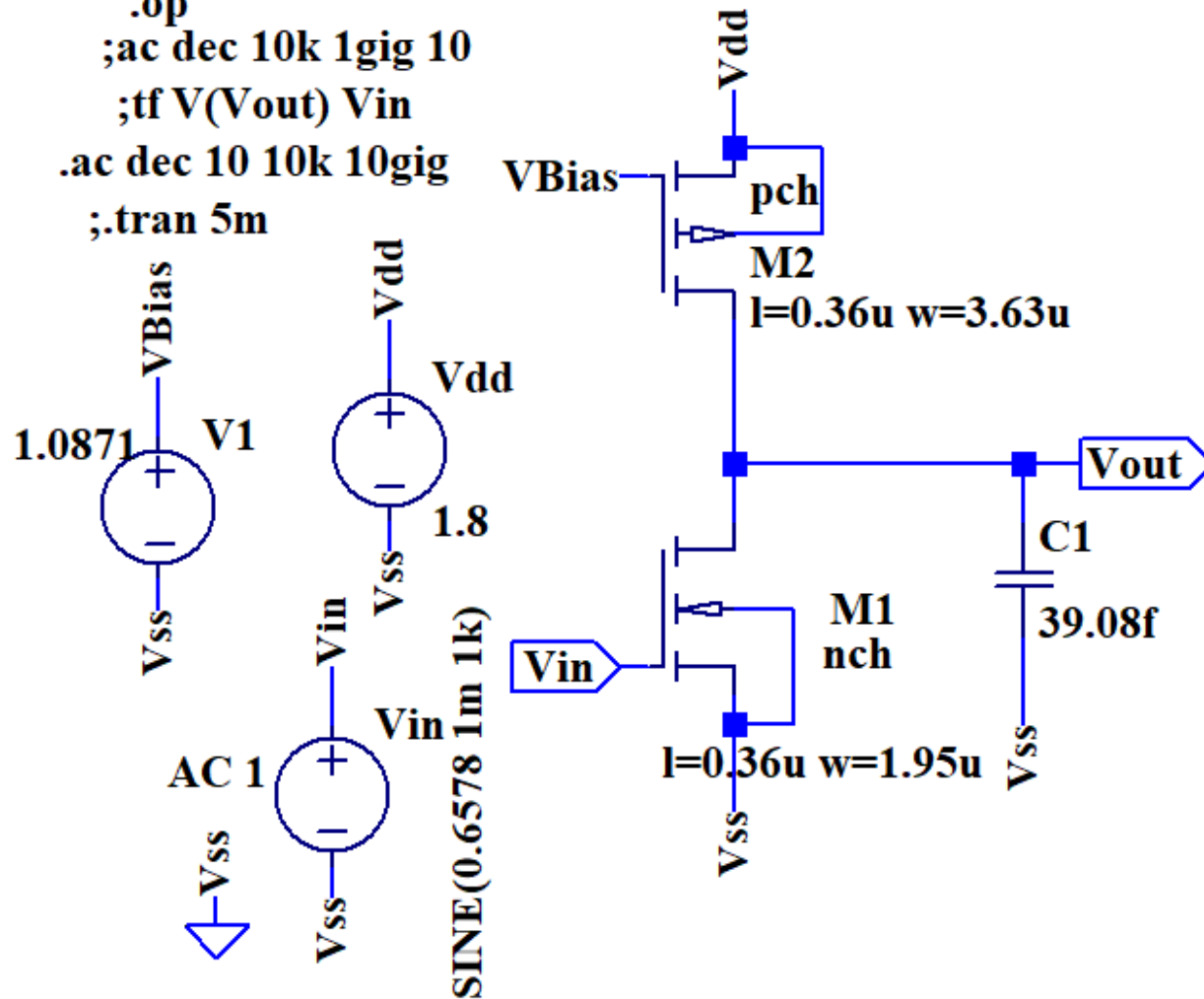
# SIMULATION

```
.include C:\Users\ASUS\Desktop\CMOS180.txt
.op
;ac dec 10k 1gig 10
;tf V(Vout) Vin
.ac dec 10 10k 10gig
;.tran 5m
```



## SOME CHANGES

Internal capacitance at node  $V_{out} = c_{gd2} + c_{gd1}(1+A_v)$

$$C(V_{out}) = 3.36 \text{ fF}$$

$$\text{So } C_L = 42.44 \text{ f} - 3.36 \text{ f} = \mathbf{39.08 \text{ fF}}$$

# RESULT AND CONCLUSION

Simulated Value	Specifications
$A_v = 40.01 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$BW = 25.06 \text{ MHz}$	$BW = 25 \text{ MHz}$
$GBW = 1.002 \text{ GHz}$	$GBW = 1 \text{ GHz}$
$R_{out} = 149.327 \text{ K}\Omega$	$R_{out} = 150 \text{ K}\Omega$
$I_d = 26.73 \text{ }\mu\text{A}$	$I_d = 26.6 \text{ }\mu\text{A}$
$V_{out(dc)} = 0.773 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$

# SPICE ERROR LOG FILE

--- Transfer Function ---


```
Transfer_function:          -40.0109          transfer
vin#Input_impedance:        1e+020           impedance
output_impedance_at_V(vout): 149327          impedance
```

Semiconductor Device Operating Points:


--- BSIM3 MOSFETS ---

Name:	m2	m1
Model:	pch	nch
Id:	-2.67e-05	2.67e-05
Vgs:	-7.13e-01	6.58e-01
Vds:	-1.03e+00	7.74e-01
Vbs:	0.00e+00	0.00e+00
Vth:	-4.48e-01	4.59e-01
Vdsat:	-2.19e-01	1.52e-01
Gm:	1.87e-04	2.68e-04
Gds:	3.21e-06	3.49e-06
Gmb	5.86e-05	7.00e-05
Cbd:	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00
Cgsov:	2.38e-15	9.57e-16
Cgdov:	2.38e-15	9.57e-16
Cgbov:	2.98e-19	3.28e-19
dQgdVgb:	1.24e-14	6.48e-15
dQgdVdb:	-2.38e-15	-9.32e-16
dQgdVsb:	-9.67e-15	-5.23e-15
dQddVgb:	-2.39e-15	-9.63e-16
dQddVdb:	2.39e-15	9.60e-16
dQddVsb:	4.60e-18	4.49e-18
dQbdVgb:	-1.61e-15	-9.88e-16
dQbdVdb:	-5.20e-19	1.92e-18
dQbdVsb:	-7.20e-16	-4.05e-16

# UNIT DEVICES

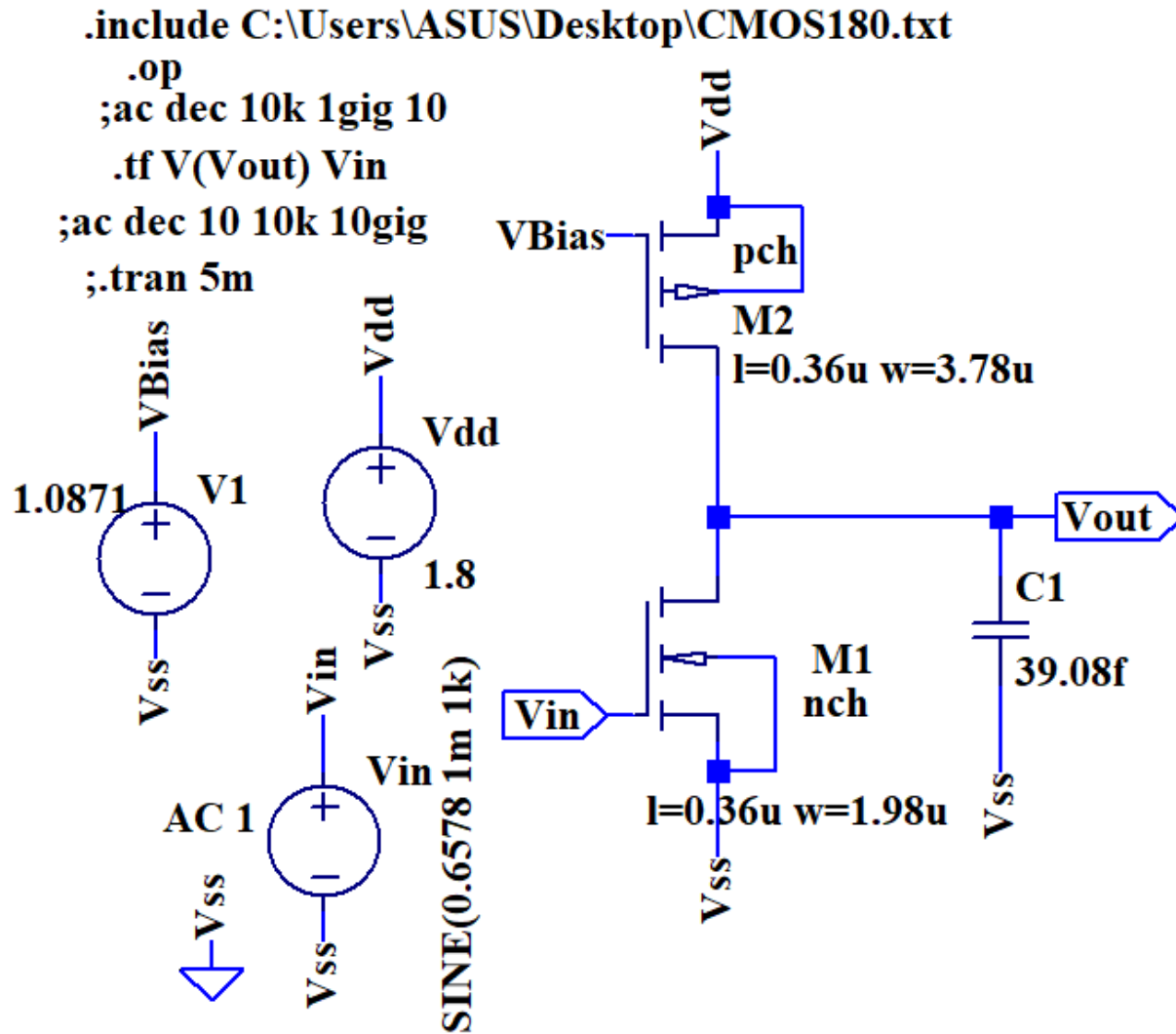

# TRANSIENT ANALYSIS

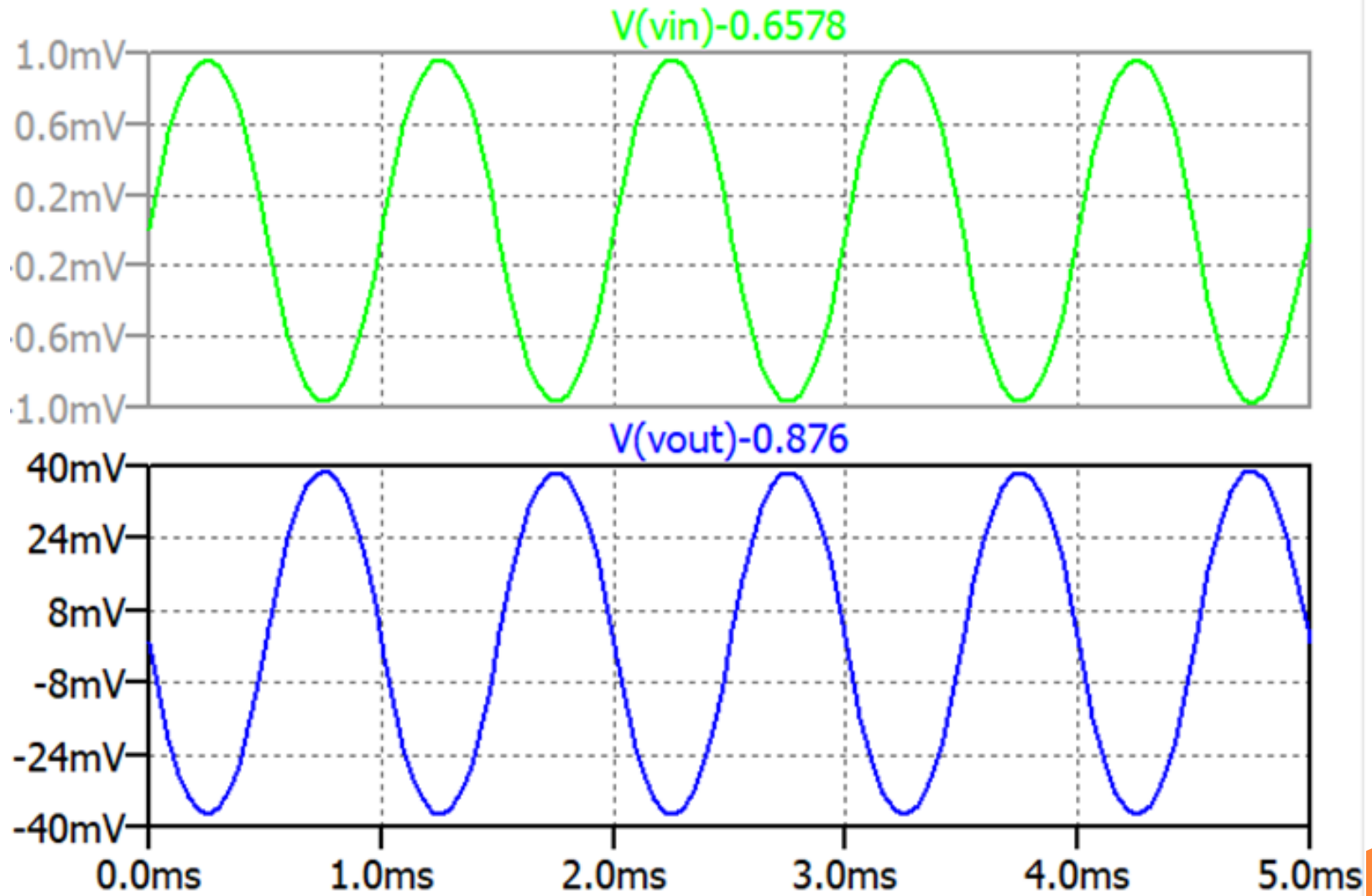


$V_{in}(p-p)=2 \text{ mV}$

$V_{out}=78.88 \text{ mV}$

Gain=39.44



# FREQUENCY


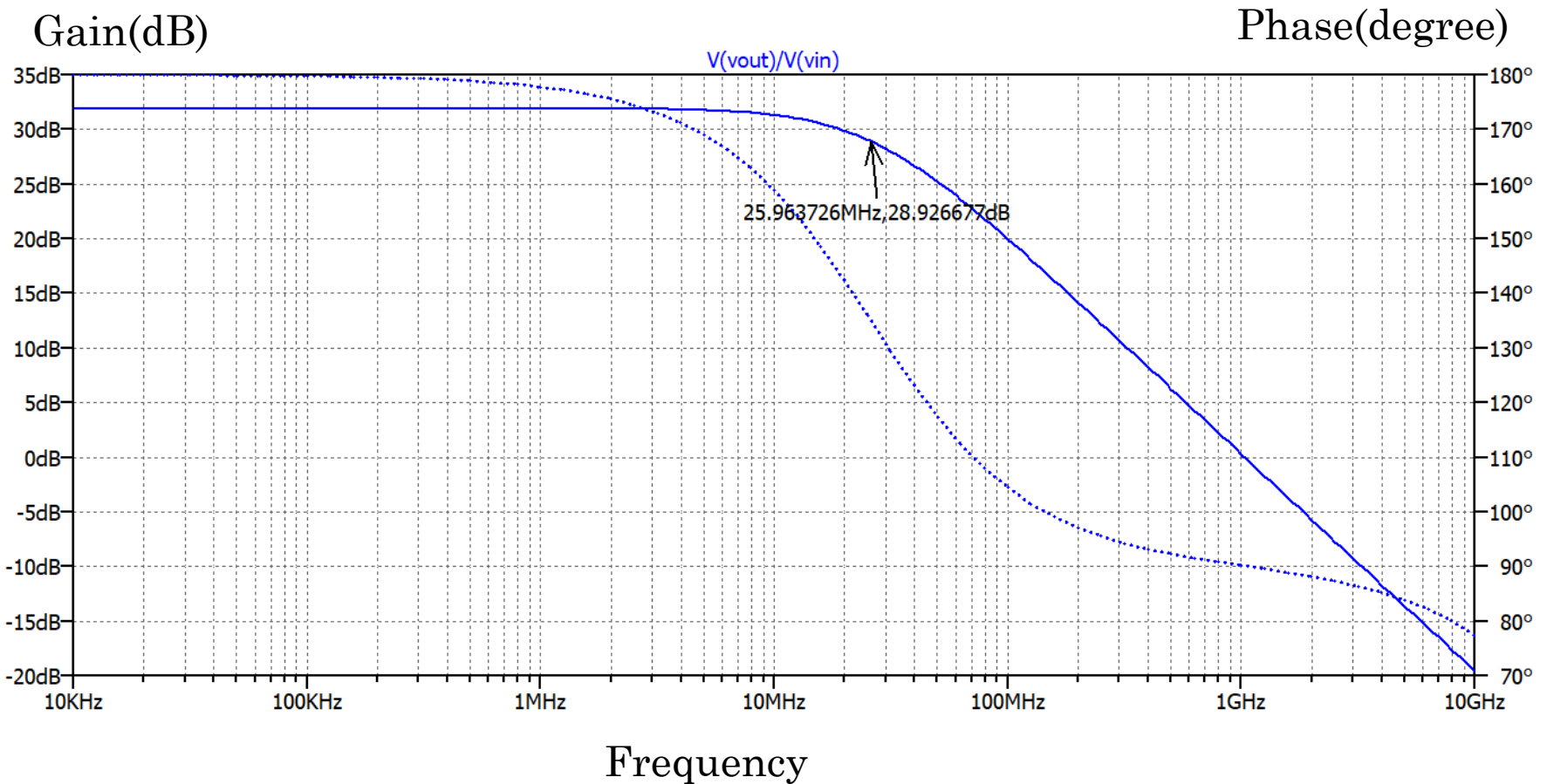


BW=25.96 MHz
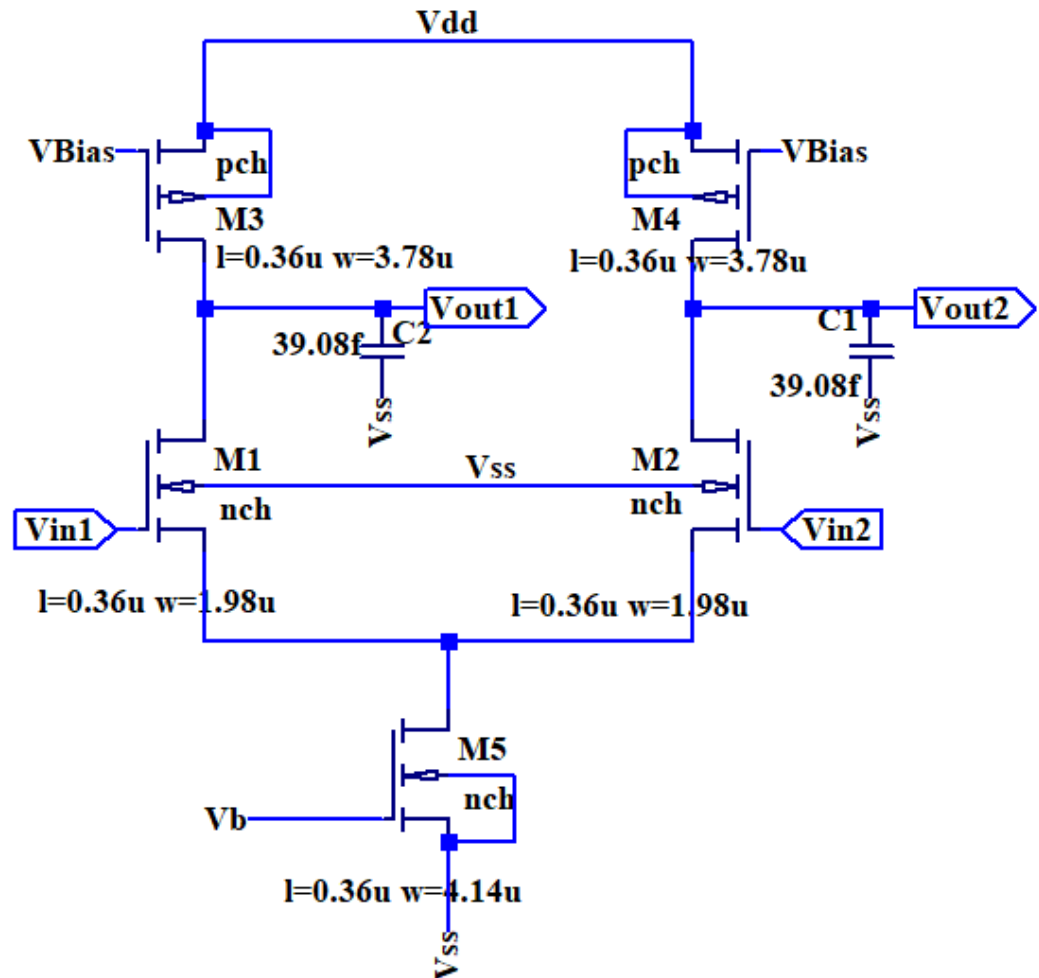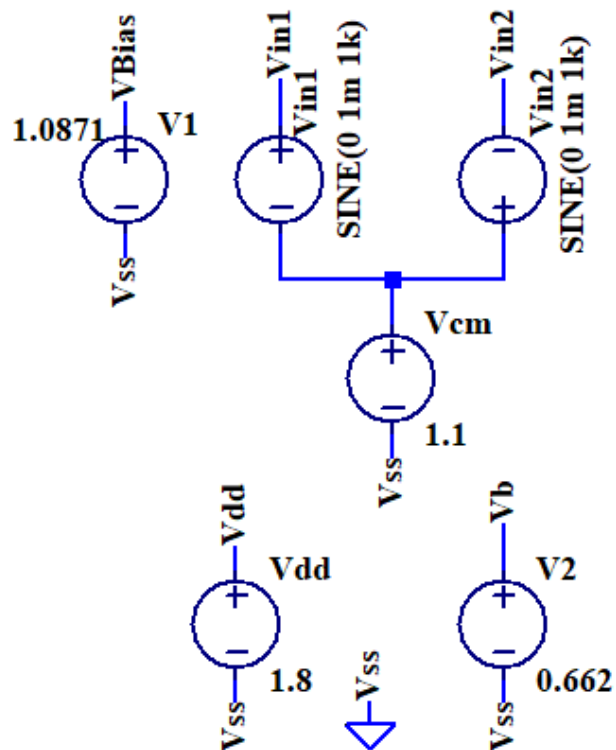
# DIFFERENTIAL PAIR

Using two Common Source Amplifier

```
.include C:\Users\ASUS\Desktop\CMOS180.txt
.op
;ac dec 10k 1gig 10
.tf V(Vout1,Vout2) (Vin1,Vin2)
;ac dec 10 10k 10gig
;tran 5m
```



# CALCULATION FOR CURRENT SOURCE

$$I_d = 54.96 \mu A$$


$$g_m/I_d = 10 \dots (\text{Choose})$$

$$V_{gs} = V_b = 0.662$$

$$I_d/w = 13.41$$

$$W_5 = 4.09 \mu m$$

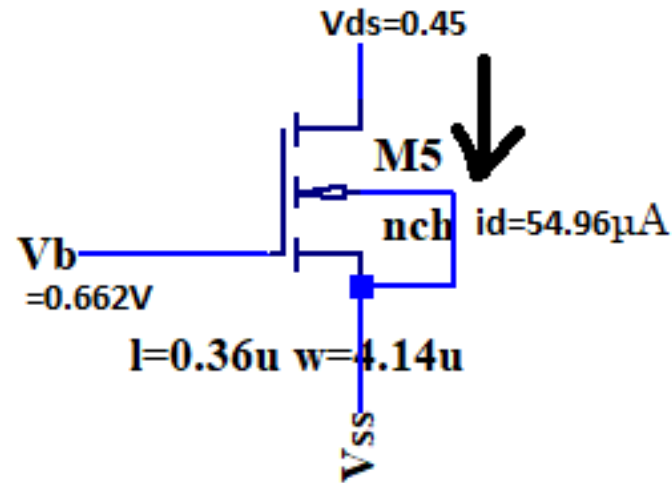
$$W_5 = 4.14 \mu m \dots \text{for unit device}$$



# RESULT AND CONCLUSION


Simulated Value	Specifications
$A_v = 36.18 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$BW = 28.66 \text{ MHz}$	$BW = 25 \text{ MHz}$
$GBW = 1.03 \text{ GHz}$	$GBW = 1 \text{ GHz}$
$R_{out} = 263.492 \text{ K}\Omega$	
$I_{ss} = 54.46 \text{ }\mu\text{A}$	$I_{ss} = 54.96 \text{ }\mu\text{A}$
$V_{out(dc)} = 0.949 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$

# TRANSIENT ANALYSIS

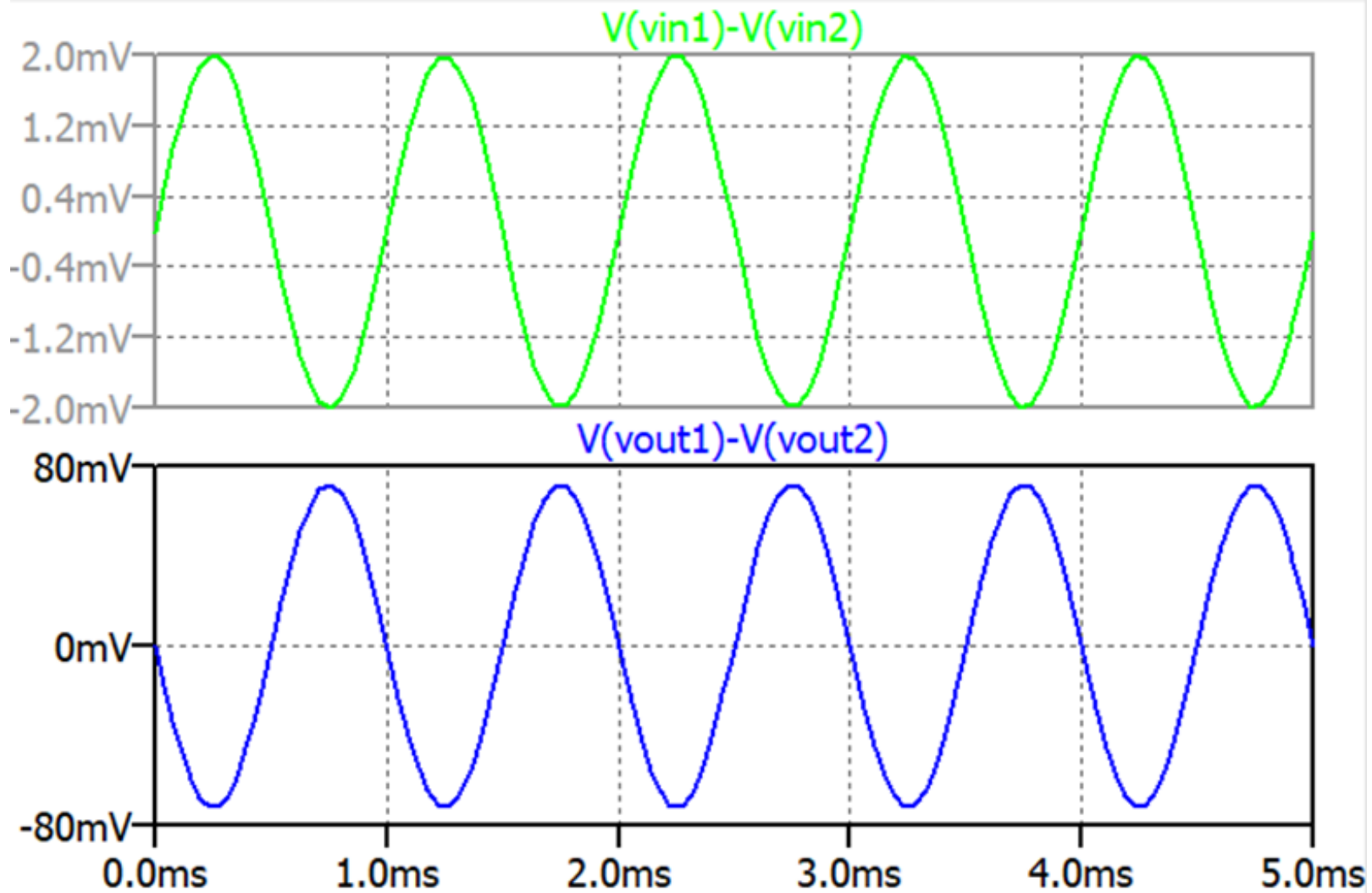

$V_{\text{in1}}-V_{\text{in2}}(\text{pp})=4 \text{ mV}$      $V_{\text{out1}}-V_{\text{out2}}(\text{pp})=144.56\text{mV}$      $\text{Gain}=36.14$

# FREQUENCY RESPONSE

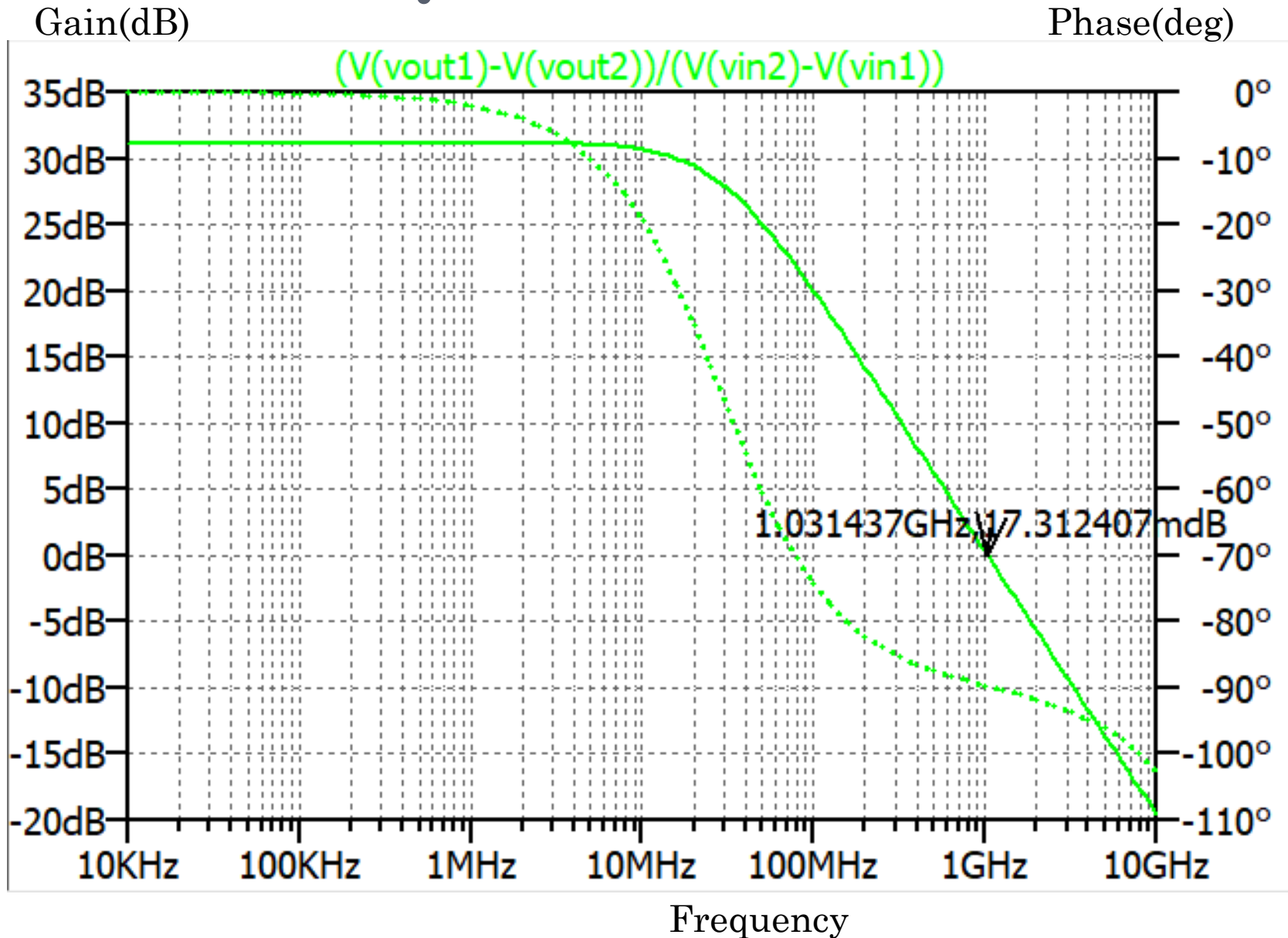

# COMMON SOURCE AMPLIFIER

**Specs:**

**$A_v=40$**

**$R_{out}=93\text{ K}\Omega$**

**Formula Used**

$$A_v = g_m \cdot R_{out}$$

$$W = \frac{I_d}{I_d/W}$$

$$R_{out} = R_{o1} \parallel R_{o3}$$

$$g_{ds} = \frac{1}{r_o}$$

- $g_m = 0.43\text{ mS}$

- $g_m/I_d = 12$

- $I_d = 35.8\text{ }\mu\text{A}$

- $R_{o1} = 165\text{ K}\Omega$

- $g_{ds3} = 4.69\text{ }\mu\text{S}$

- $(I_d/g_{ds})_3 = 7.63$

- $g_m/I_d = 6.315$

- $W_3 = 3.91\text{ }\mu\text{m}$

$$g_m/g_{ds} = 70.92$$

$$g_{ds} = 6.06\text{ }\mu\text{S}$$

$$R_{o3} = 213.125\text{ K}\Omega$$

$$I_d/W = 9.896$$


$$W_1 = 3.61\text{ }\mu\text{m}$$

$$I_d/W = 9.133$$

# SIMULATION

**.include C:\Users\ASUS\Desktop\CMOS180.txt**

**.tf V(Vout) Vin**

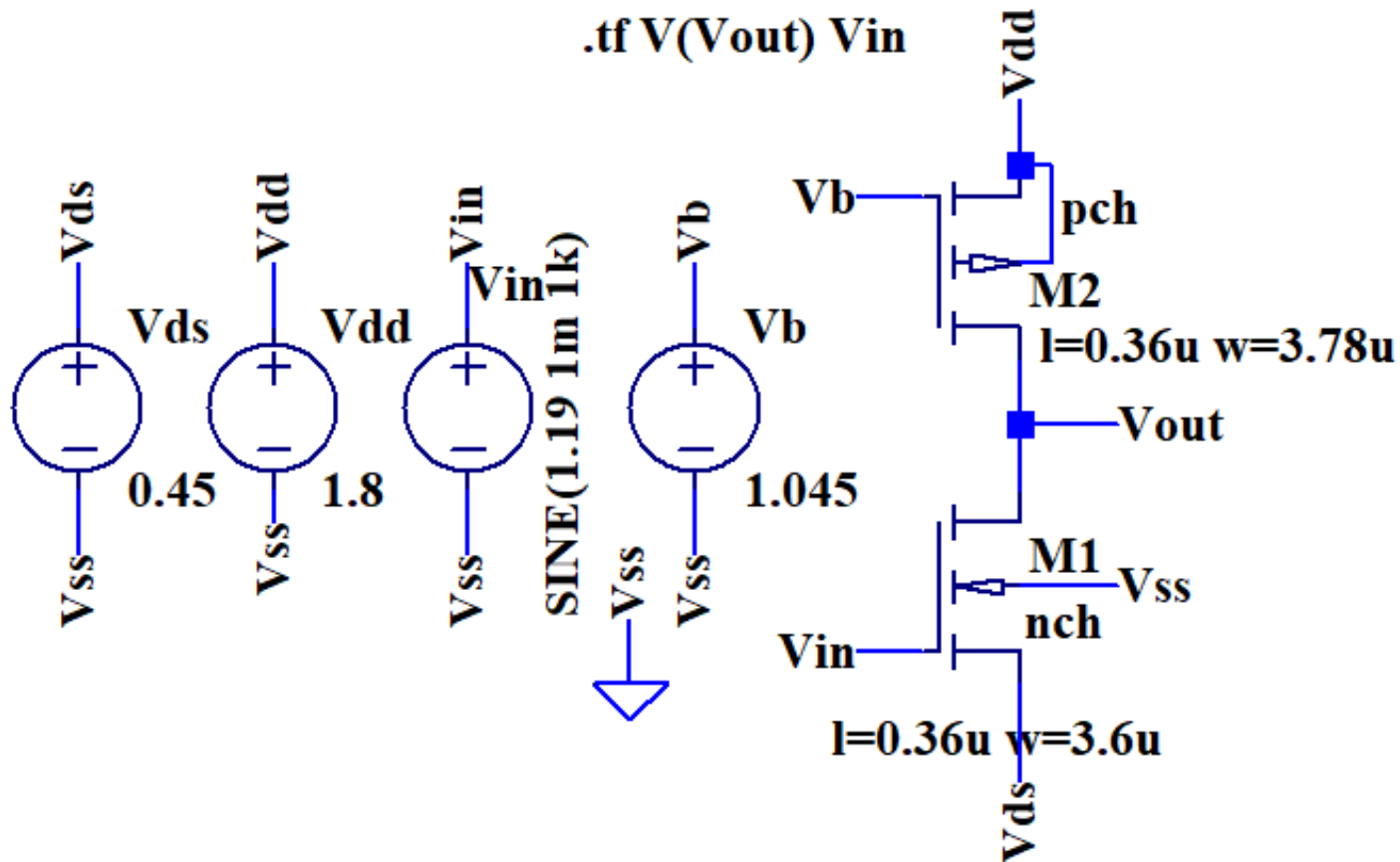




# RESULTS

Simulated Value	Specifications
$A_v = 40.15 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$R_{out} = 95.632 \text{ K}\Omega$	$R_{out} = 93 \text{ K}\Omega$
$I_d = 35.18 \text{ }\mu\text{A}$	$I_d = 35.8 \text{ }\mu\text{A}$
$V_{out(dc)} = 1.07 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$

# OP-AMP (STAGE-1)


## Using Common Source Amplifier

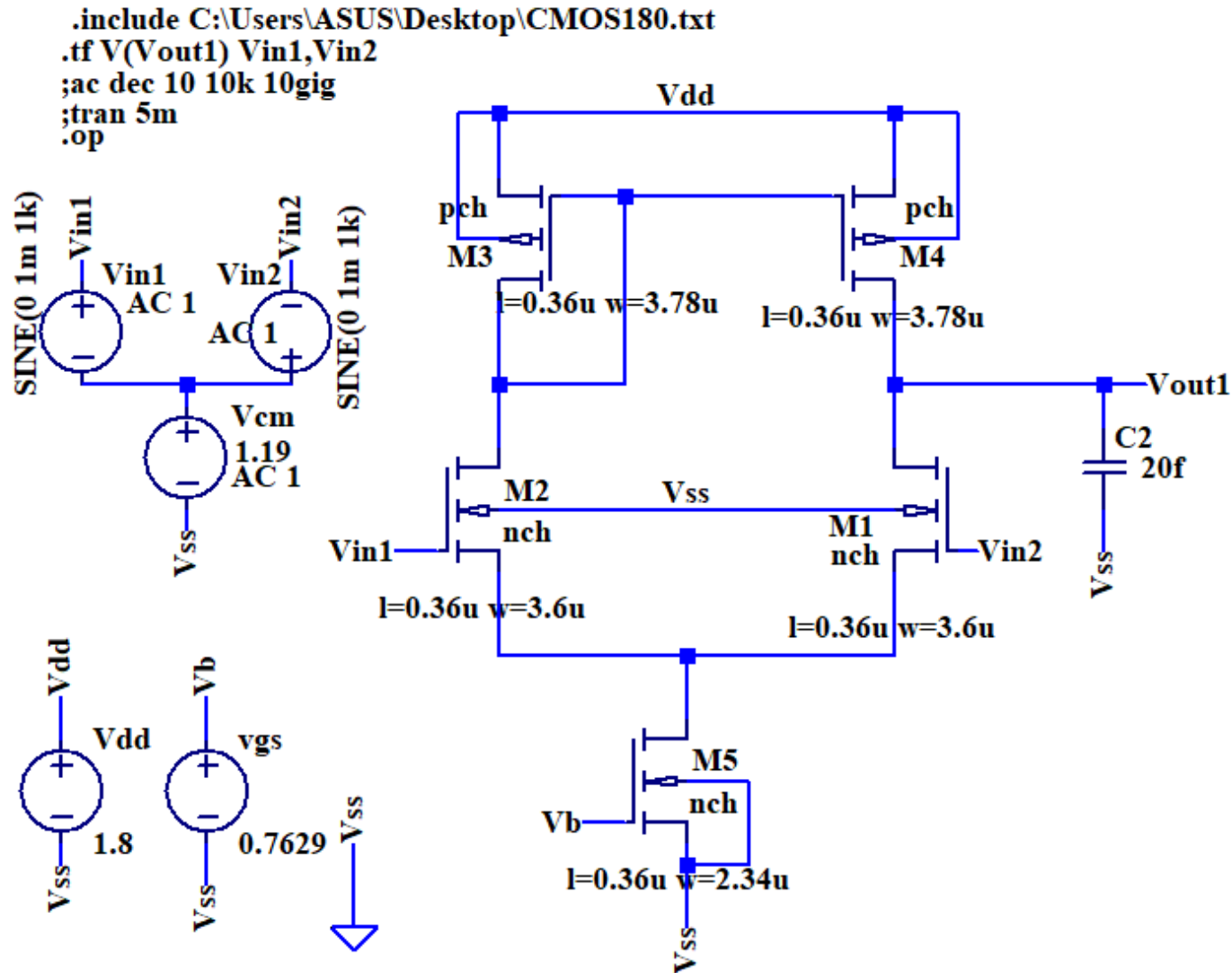

# RESULT


Simulated Value	Specifications
$A_v = 39.8092 \text{ v/v}$	$A_v = 40 \text{ v/v}$
$BW = 28.66 \text{ MHz}$	$BW = 25 \text{ MHz}$
$GBW = 1.03 \text{ GHz}$	$GBW = 1 \text{ GHz}$
$R_{out} = 97.259 \text{ K}\Omega$	$R_{out} = 93 \text{ K}\Omega$
$I_{ss} = 70.3 \text{ }\mu\text{A}$	$I_{ss} = 71.6 \text{ }\mu\text{A}$
$V_{out(dc)} = 1.04 \text{ V}$	$V_{out(dc)} = 1.15 \text{ V}$

# FREQUENCY ANALYSIS

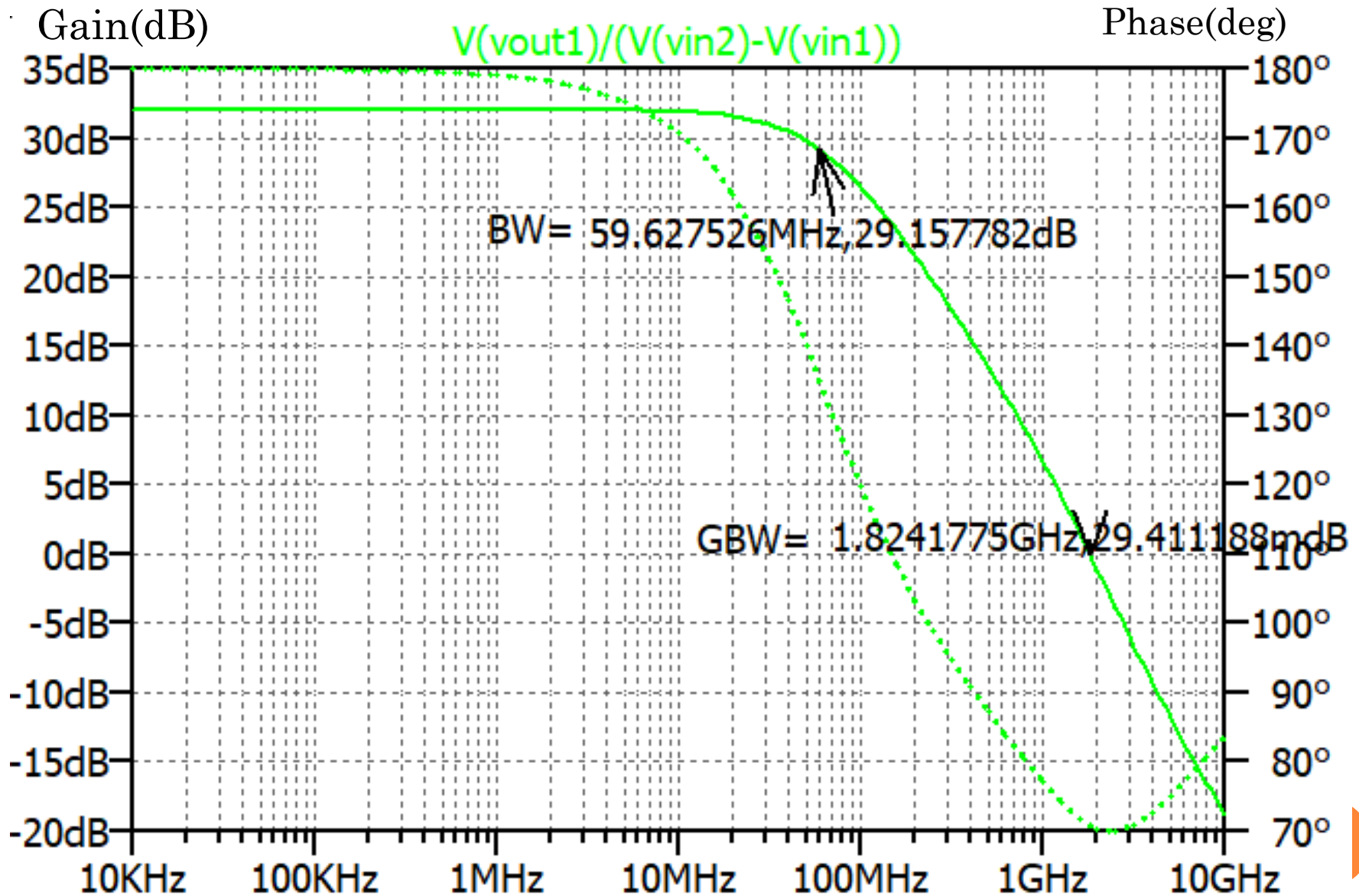

Frequency

# TRANSIENT ANALYSIS

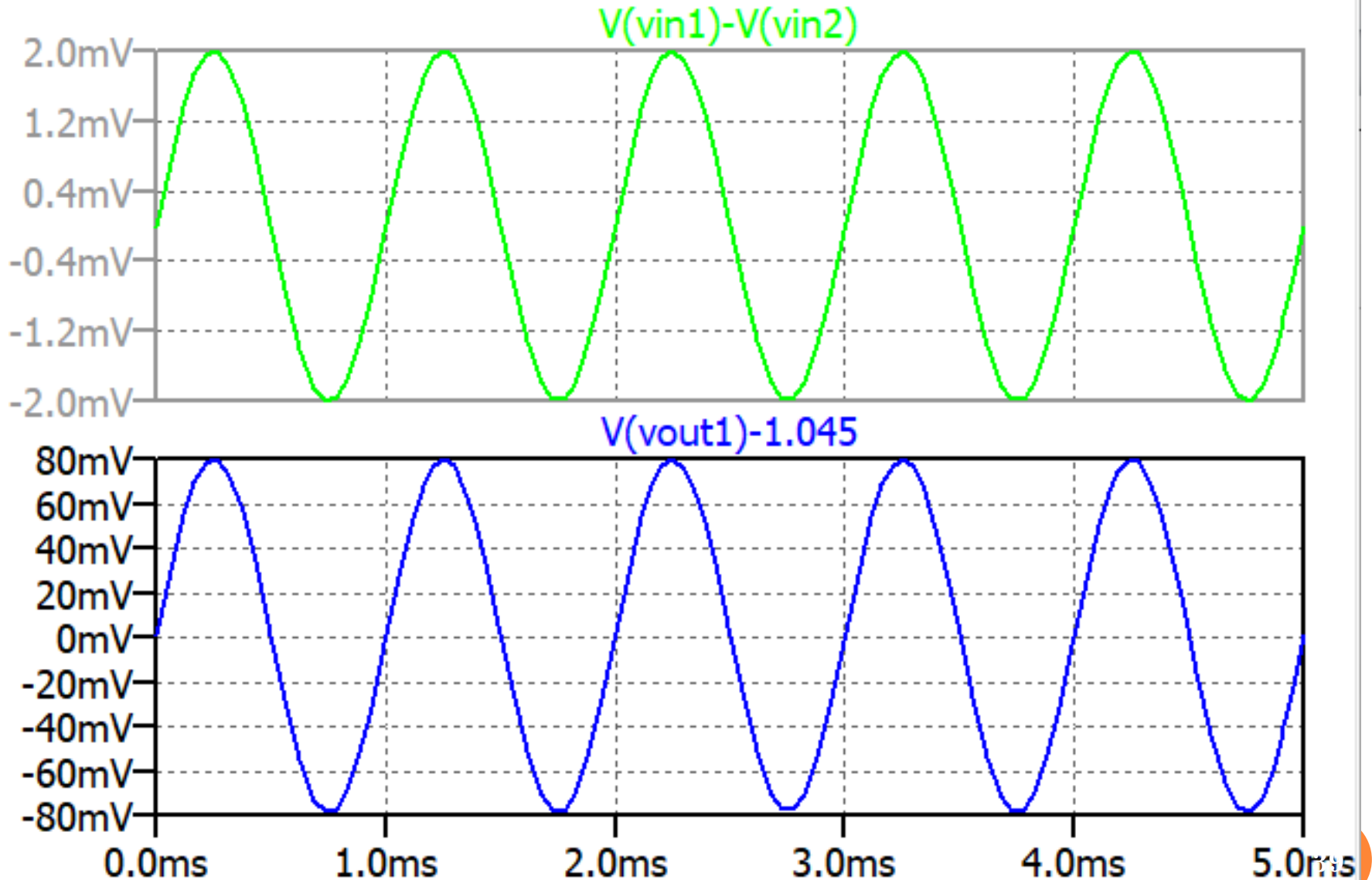

$V_{\text{in1}}-V_{\text{in2}}(\text{pp})=4 \text{ mV}$      $V_{\text{out1}}(\text{pp})=158.68 \text{ mV}$      $\text{Gain}=39.67$

# COMMON SOURCE AMPLIFIER

## For Second Stage op-amp

**Specs:**

$$A_v = 28$$

$$g_{m2} = 8 \times 0.432 \text{ mS} = 3.384 \text{ mS}$$

$$R_{out2} = 8 \text{ K}\Omega$$

- $V_{gs1} = 780 \text{ mV}$

- $g_m/id = 5.466$        $id/w = 11.9$  ....from chart

- $g_m/g_{ds} = 46.96$  ....from chart

- $I_d = 619 \text{ }\mu\text{A}$

- $W_6 = 52 \text{ }\mu\text{m}$

- $g_{ds6} = 72.06 \text{ }\mu\text{S}$        $R_{o6} = 13.87 \text{ K}\Omega$

- $R_{o7} = 18.9 \text{ K}\Omega$        $g_{ds7} = 52.9 \text{ }\mu\text{S}$

- $(I_d/g_{ds})_7 = 11.7$
- $g_m/i_d = 6.24$        $i_d/w = 31.05$
- $W_7 = 19.9 \mu\text{m}$        **$W_7 = 15.84 \mu\text{m}$  in Simulation**
- $V_{gs7} = 0.7629 \text{ V}$

# SIMULATION


```
.include C:\Users\ASUS\Desktop\CMOS180.txt
```

```
.tf V(Vout) Vin
```

```
;ac dec 10 10k 10gig
```

```
;tran 5m
```

```
.op
```

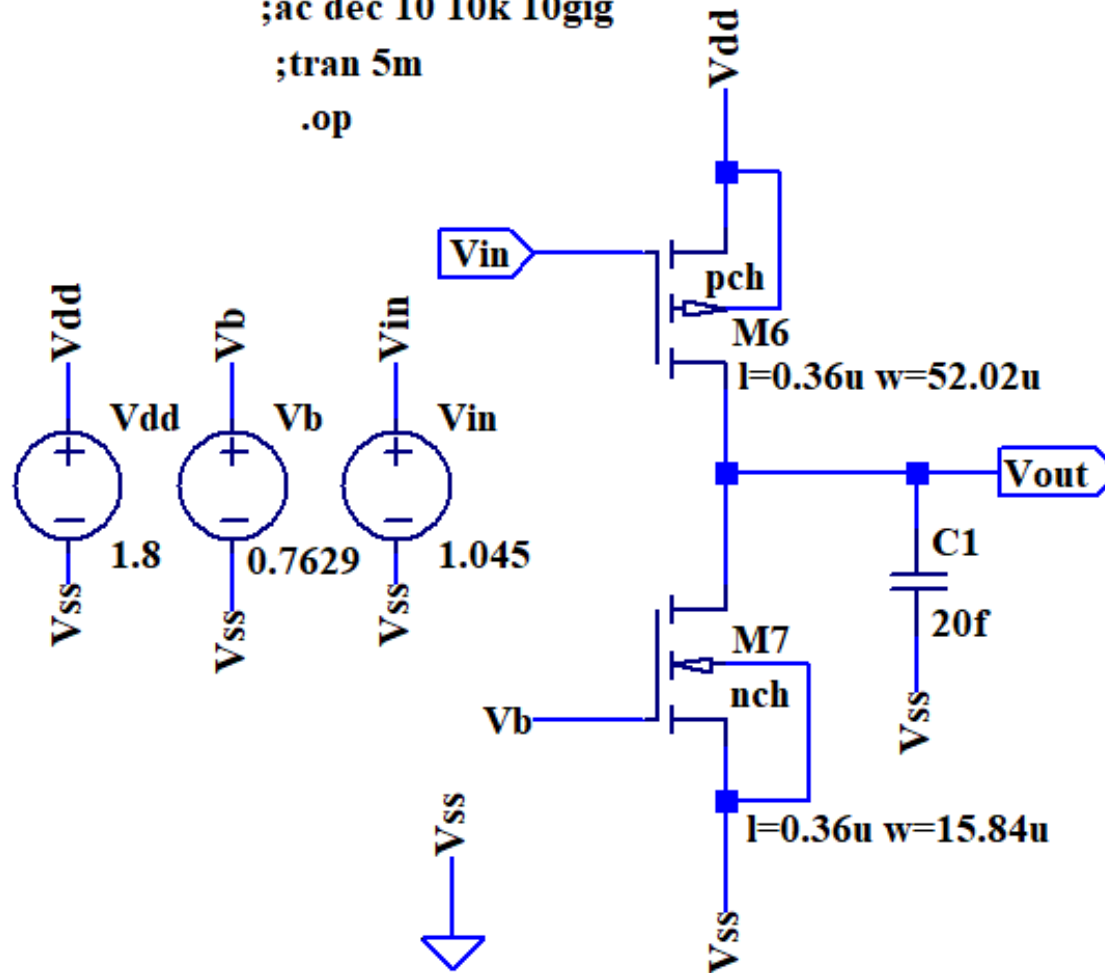





# RESULT

Simulated Value	Specifications
$A_v = 28.34 \text{ v/v}$	$A_v = 28 \text{ v/v}$
$BW = 256.9 \text{ MHz}$	
$GBW = 9.24 \text{ GHz}$	
$R_{out} = 9.6 \text{ K}\Omega$	$R_{out} = 8 \text{ K}\Omega$
$I_{B2} = 494 \text{ }\mu\text{A}$	$I_{B2} = 619 \text{ }\mu\text{A}$
$V_{out(dc)} = 0.998 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$

# FREQUENCY RESPONSE

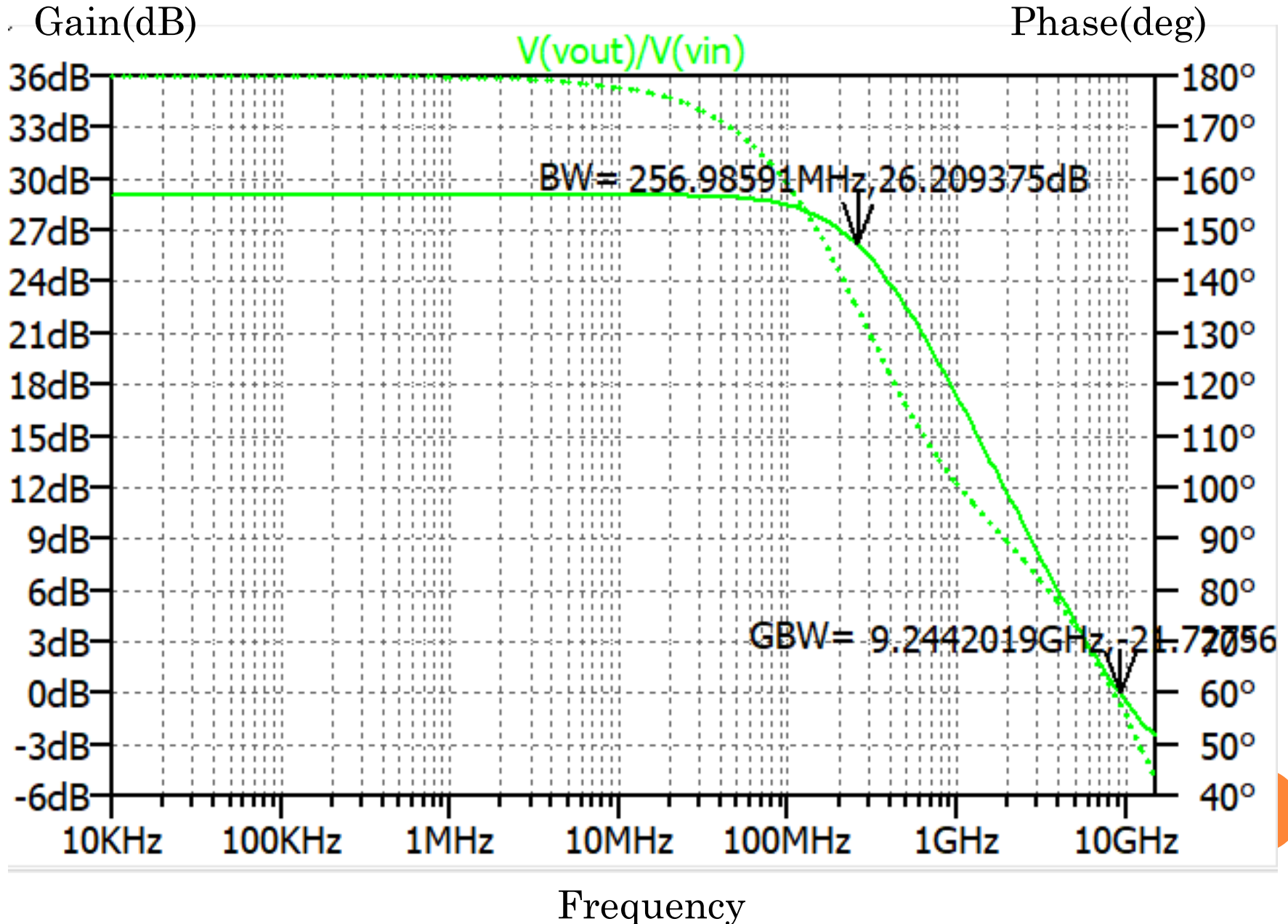

# TRANSIENT ANALYSIS

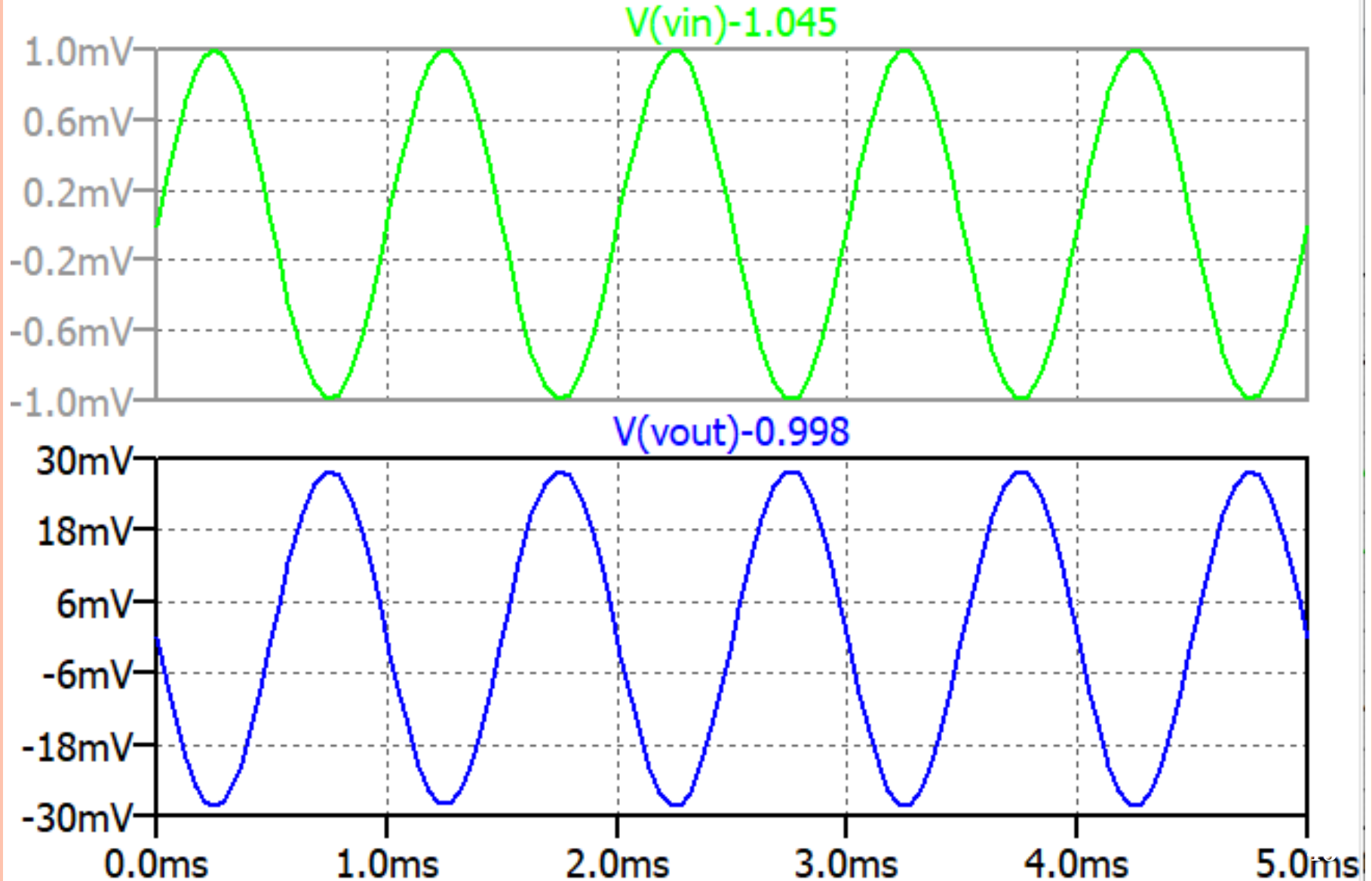

$V_{in(pp)}=2 \text{ mV}$     $V_{out(pp)}=56.63 \text{ mV}$    Gain=28.315


# PROJECT: DESIGNING OF TWO STAGE OPERATIONAL AMPLIFIER

## Specification


Gain( $A_v$ )	$\geq 1000$ (60dB)
GBW	1GHz
Phase Margin	$\geq 50$
Load Capacitance	20 fF

# PROJECT: TWO STAGE OP-AMP

## Combining Stage-1 and Stage-2

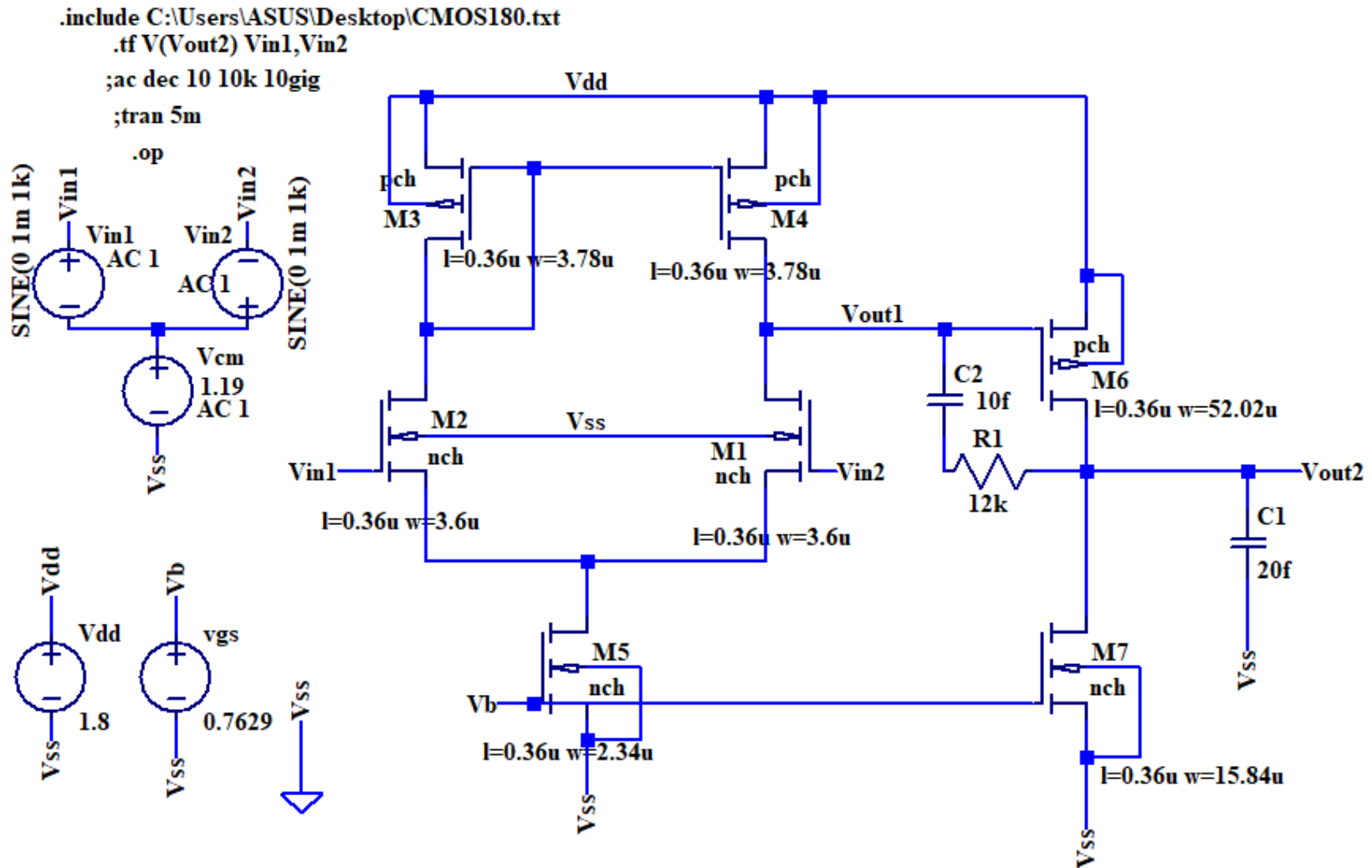

# CAPACITOR

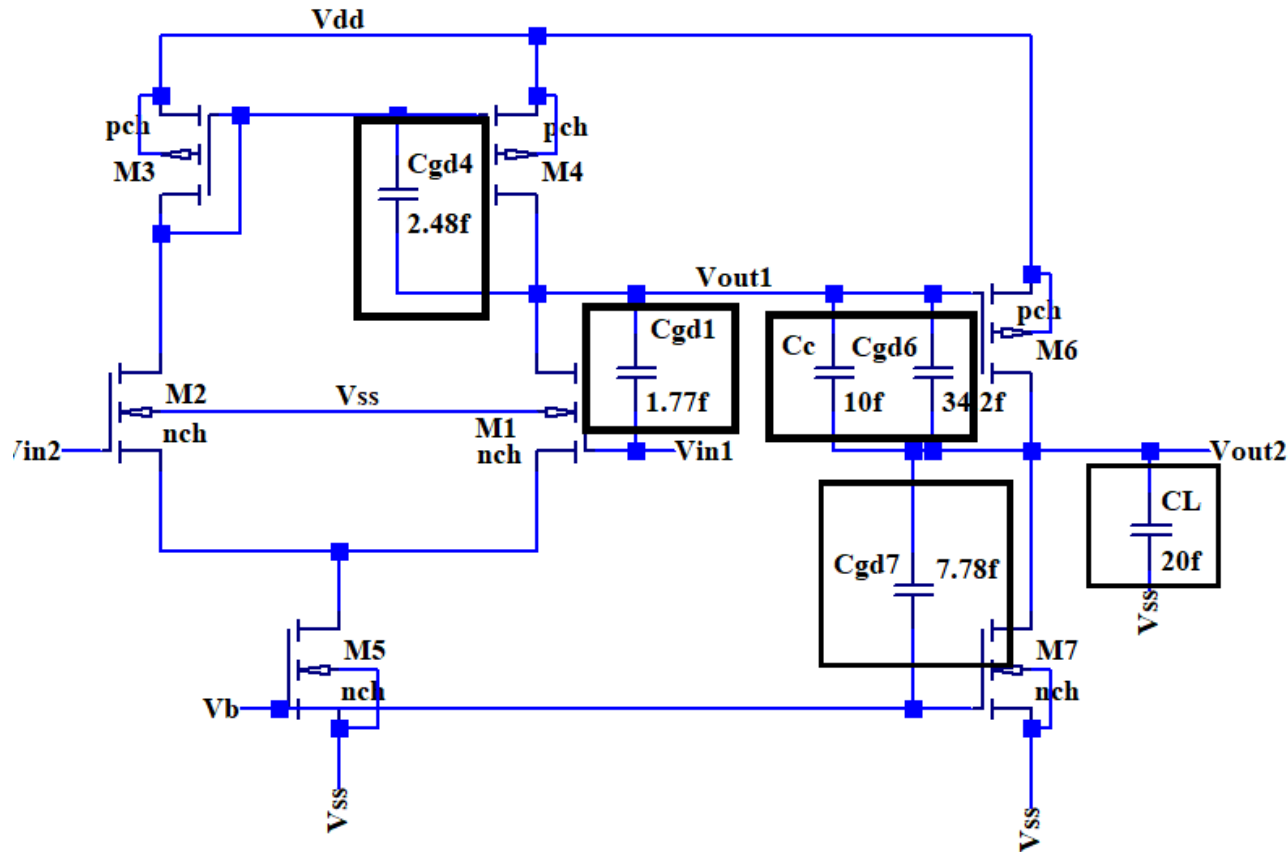

$C1 = \text{Capacitance at Node}(V_{out1}) = C_{gd4} + C_{gd1} + \{ (C_{gd6} + C_c) * (1 + A_{v2}) \}$

$C1 = 1.3 \text{ pF}$

$C2 = \text{Capacitance at Node}(V_{out2}) = C_L + C_{gd7} + \{ (C_{gd6} + C_c) * (1 + \frac{1}{A_{v2}}) \}$

$C2 = 73.52 \text{ fF}$

# POLE AND ZERO

- Dominant Pole

- $F_{p1} = \frac{1}{2\pi \cdot R_{out1} \cdot C1}$

- $F_{p1} = 1.2 \text{ MHz}$  where  $R_{out1} = 97.25 \text{ K}\Omega$

- $F_{p2} = \text{Beyond } 1\text{GHz}$

- $S_z = \frac{1}{C_c \left( \frac{1}{G_{m6}} - R_z \right)}$

- $F_z = -1.36\text{GHz}$  where  $R_z = 12\text{k}$ ,  $G_{m2} = 2.95\text{mS}$

# FREQUENCY COMPENSATION

- $C_c = 10 \text{ fF}$  (generally  $C_c = (0.3 - 0.5) * C_L$ )
- $R_z = 12 \text{ K}\Omega$  (generally  $R_z = 1 / G_{m2}$ )
- But we have taken  $12 \text{ K}\Omega$  for achieving Phase Margin of  $45^\circ$ .



# RESULT

Simulated Value	Specifications
$A_v = 1139 \text{ v/v}$	$A_v \geq 1000 \text{ v/v}$
$BW = 1.12 \text{ MHz}$	$BW = 1 \text{ MHz}$
<b><math>GBW = 1.02 \text{ GHz}</math></b>	<b><math>GBW = 1 \text{ GHz}</math></b>
$R_{out} = 9.68 \text{ K}\Omega$	$R_{out} = 8 \text{ K}\Omega$
$V_{out(dc)} = 0.97 \text{ V}$	$V_{out(dc)} = 0.9 \text{ V}$
$I_{B1} = 70.3 \text{ }\mu\text{A}$ , $I_{B2} = 493.24 \text{ }\mu\text{A}$ Total Current = $563.54 \text{ }\mu\text{A}$ $V_{dd} = 1.8$ Power Dissipation = $1.01 \text{ mW}$	- - - -
Phase Margin = $45^\circ$	Phase Margin = $50^\circ$
Gain Margin = $16.5 \text{ dB}$	-
$C_L = 20 \text{ fF}$	$C_L = 20 \text{ fF}$

# TABLE

Stage 1	Stage 2
$L=0.36\mu\text{m}$	$L=0.36\mu\text{m}$
$W_{1,2} = 3.6\mu\text{m}$ $\frac{W}{L} = 10$	$W_6=52.02\mu\text{m}$ $\frac{W}{L} = 144.5$
$gm_{1,2} = 0.419 \text{ mS}$	$gm_6 = 2.59 \text{ mS}$
$W_{3,4} = 3.78\mu\text{m}$ $\frac{W}{L} = 10.5$	$W_7= 15.84 \mu\text{m}$ $\frac{W}{L} = 44$
$gm_{3,4} = 0.21 \text{ mS}$	$gm_7 = 3.05 \text{ mS}$

# SPICE ERROR LOG FILE

---

Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---


Name:	m6	m3	m4	m7	m5	m2	m1
Model:	pch	pch	pch	nch	nch	nch	nch
Id:	-4.93e-04	-3.52e-05	-3.52e-05	4.93e-04	7.03e-05	3.52e-05	3.52e-05
Vgs:	-7.54e-01	-7.54e-01	-7.54e-01	7.63e-01	7.63e-01	7.40e-01	7.40e-01
Vds:	-8.26e-01	-7.54e-01	-7.54e-01	9.74e-01	4.50e-01	5.96e-01	5.96e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	-4.50e-01	-4.50e-01
Vth:	-4.50e-01	-4.48e-01	-4.48e-01	4.58e-01	4.62e-01	5.82e-01	5.82e-01
Vdsat:	-2.55e-01	-2.50e-01	-2.50e-01	2.19e-01	2.15e-01	1.38e-01	1.38e-01
Gm:	2.95e-03	2.11e-04	2.11e-04	3.05e-03	4.40e-04	4.19e-04	4.19e-04
Gds:	6.24e-05	4.69e-06	4.69e-06	4.09e-05	1.09e-05	5.73e-06	5.73e-06
Gmb:	9.53e-04	6.66e-05	6.66e-05	7.91e-04	1.13e-04	9.52e-05	9.52e-05
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	3.42e-14	2.48e-15	2.48e-15	7.78e-15	1.15e-15	1.77e-15	1.77e-15
Cgdov:	3.42e-14	2.48e-15	2.48e-15	7.78e-15	1.15e-15	1.77e-15	1.77e-15
Cgbov:	2.98e-19	2.98e-19	2.98e-19	3.28e-19	3.28e-19	3.28e-19	3.28e-19
dQgdVgb:	1.78e-13	1.30e-14	1.30e-14	5.26e-14	7.80e-15	1.18e-14	1.18e-14
dQgdVdb:	-3.42e-14	-2.48e-15	-2.48e-15	-7.58e-15	-1.13e-15	-1.72e-15	-1.72e-15
dQgdVsb:	-1.38e-13	-1.01e-14	-1.01e-14	-4.27e-14	-6.32e-15	-9.53e-15	-9.53e-15
dQddVgb:	-3.43e-14	-2.50e-15	-2.50e-15	-7.81e-15	-1.19e-15	-1.78e-15	-1.78e-15
dQddVdb:	3.43e-14	2.49e-15	2.49e-15	7.79e-15	1.18e-15	1.78e-15	1.78e-15
dQddVsb:	1.04e-16	8.68e-18	8.68e-18	2.36e-17	1.14e-17	1.33e-17	1.33e-17
dQbdVgb:	-2.25e-14	-1.67e-15	-1.67e-15	-7.92e-15	-1.17e-15	-1.67e-15	-1.67e-15
dQbdVdb:	-2.52e-17	-2.70e-18	-2.70e-18	1.63e-17	-9.51e-18	7.38e-19	7.38e-19
dQbdVsb:	-1.10e-14	-7.45e-16	-7.45e-16	-3.25e-15	-4.67e-16	-4.71e-16	-4.71e-16

---


--- Transfer Function ---

Transfer_function:	-1139.14	transfer	
vin1#Input_impedance:	1e+020	impedance	
output_impedance_at_V(vout2):		9688.45	impedance

# FREQUENCY RESPONSE

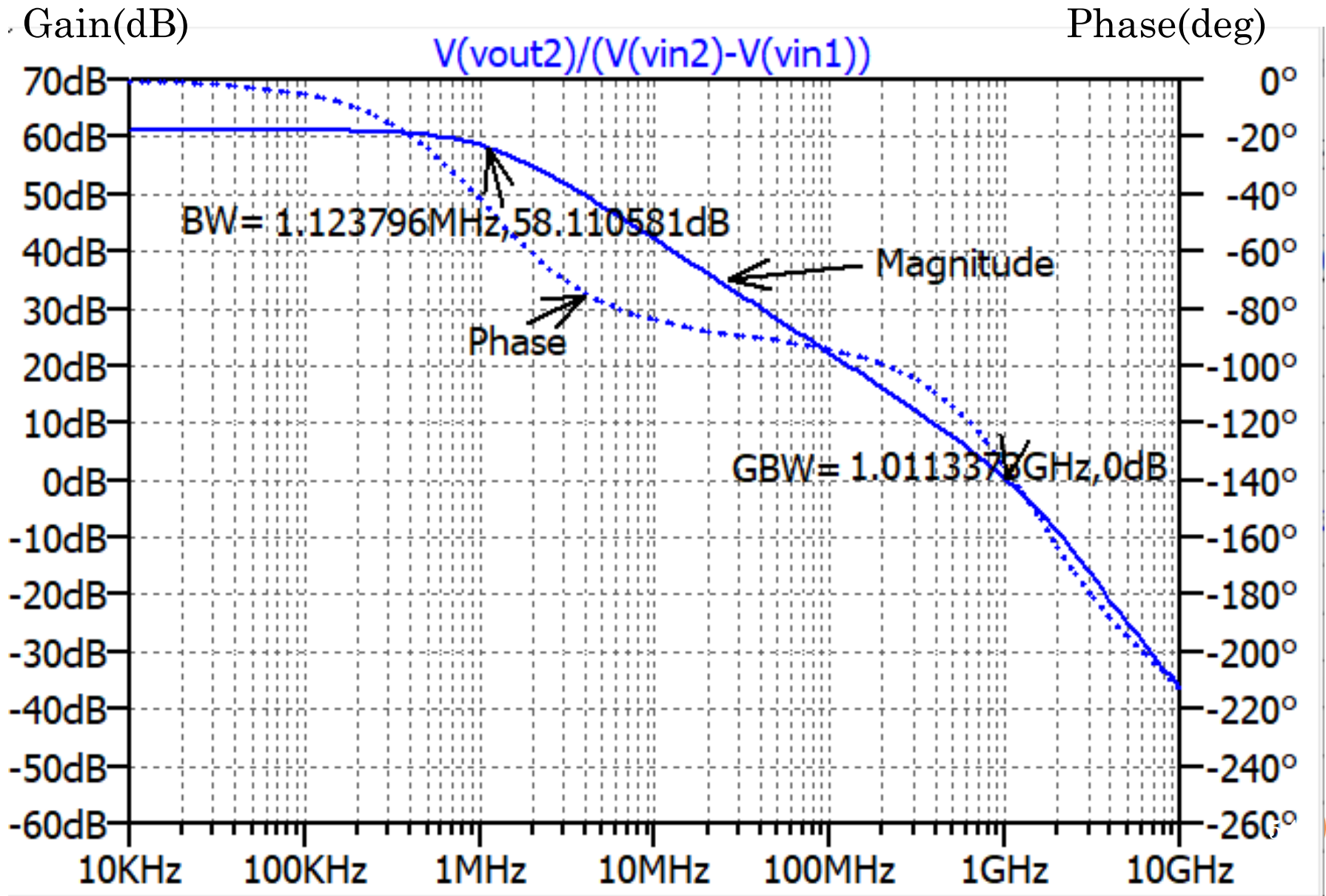

# TRANSIENT ANALYSIS

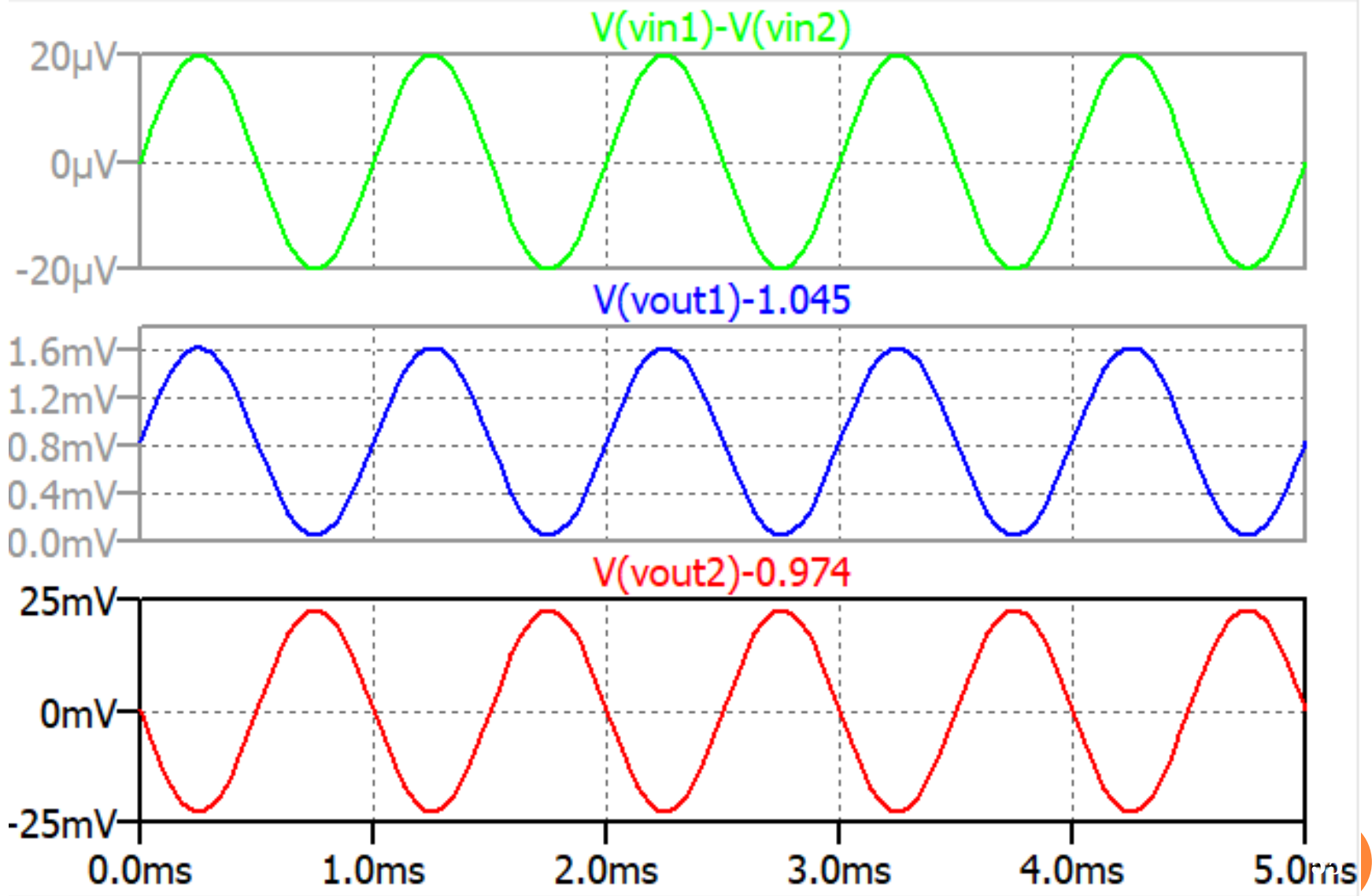

$V_{\text{in1}}-V_{\text{in2}}(\text{pp})=40\mu\text{V}$      $V_{\text{out2}}(\text{pp})=45.54\text{mV}$     Gain=1138.5